

float_add.v

```
module float_add (
    input [7:0] aIn,
    input [7:0] bIn,
    output reg [7:0] result
);

wire [7:0] big_aOut, big_bOut;

big_number_first step1 (
    .aIn(aIn),
    .bIn(bIn),
    .aOut(big_aOut),
    .bOut(big_bOut)
);

wire [2:0] aExp;
wire [4:0] aMan;
wire [2:0] bExp;
wire [4:0] bMan;

assign aExp = big_aOut[7:5];
assign aMan = big_aOut[4:0];
assign bExp = big_bOut[7:5];
assign bMan = big_bOut[4:0];

wire [2:0] distance1;
assign distance1 = aExp - bExp;

wire [2:0] bExpShift;
wire [4:0] bManShift;

assign bExpShift = bExp +
distance1;

shifter step2 (
    .in(bMan),
    .distance(distance1),
    .direction(1'b1),
    .out(bManShift)
);

wire [4:0] adderSum;
wire adderCout;

adder step3 (
    .A(aMan),
    .B(bManShift),
    .S(adderSum),
    .Cout(adderCout)
);

wire [2:0] distance2;
assign distance2 = {2'b00,
adderCout};

wire [2:0] resultExp;
wire [4:0] resultMan;

assign resultExp = bExpShift +
adderCout;

shifter step4 (
    .in(adderSum),
    .distance(distance2),
    .direction(1'b1),
    .out(resultMan)
);

always @* begin
    if(bExpShift == 3'b111 &&
adderCout == 1'b1)
        result = 8'b11111111;
    else
        begin
            case(adderCout)
                1'b0: result =
{resultExp, resultMan};
                1'b1: result =
{resultExp, 1'b1,
resultMan[3:0]};
            endcase
        end
end

endmodule
```

big_number_first.v

```
module big_number_first (
    input [7:0] aIn,
    input [7:0] bIn,
    output reg [7:0] aOut,
    output reg [7:0] bOut
);

wire [2:0] aExp;
wire [4:0] aMan;
wire [2:0] bExp;
wire [4:0] bMan;

assign aExp = aIn[7:5];
assign aMan = aIn[4:0];
assign bExp = bIn[7:5];
assign bMan = bIn[4:0];

always @* begin
    if((aExp < bExp) || (aExp ==
bExp && aMan < bMan))
        begin
            aOut = {bExp, bMan};
            bOut = {aExp, aMan};
        end
    else
        begin
            aOut = {aExp, aMan};
            bOut = {bExp, bMan};
        end
end

endmodule
```

shifter.v

```
module shifter (
    input [4:0] in,
    input [2:0] distance,
    input direction,
    output reg [4:0] out
);

always @* begin
    case(direction)
        1'b0: out = in << distance;
        1'b1: out = in >> distance;
    endcase
end

endmodule
```

adder.v

```
module adder(  
    input [4:0] A,  
    input [4:0] B,  
    output [4:0] S,  
    output Cout  
);  
  
wire Cin = 1'b0;  
wire Cout0;  
wire Cout1;  
wire Cout2;  
wire Cout3;  
  
fullAdder a0 (  
    .A(A[0]),  
    .B(B[0]),  
    .Cin(Cin),  
    .Cout(Cout0),  
    .S(S[0])  
);  
  
fullAdder a1 (  
    .A(A[1]),  
    .B(B[1]),  
    .Cin(Cout0),  
    .Cout(Cout1),  
    .S(S[1])  
);  
  
fullAdder a2 (  
    .A(A[2]),  
    .B(B[2]),  
    .Cin(Cout1),  
    .Cout(Cout2),  
    .S(S[2])  
);  
  
fullAdder a3 (  
    .A(A[3]),  
    .B(B[3]),  
    .Cin(Cout2),  
    .Cout(Cout3),  
    .S(S[3])  
);
```

```
fullAdder a4 (  
    .A(A[4]),  
    .B(B[4]),  
    .Cin(Cout3),  
    .Cout(Cout),  
    .S(S[4])  
);
```

```
endmodule
```

fullAdder.v

```
module fullAdder (  
    input A,  
    input B,  
    input Cin,  
    output S,  
    output Cout  
);  
  
wire AxB;  
assign AxB = A ^ B;  
  
wire AxBaCin;  
assign AxBaCin = (A ^ B) & Cin;  
  
wire AaB;  
assign AaB = A & B;  
  
assign Cout = AaB | AxBaCin;  
assign S = AxB ^ Cin;  
  
endmodule
```

float_add_tb.v

```
module float_add_tb ();

    reg [7:0] sim_aIn;
    reg [7:0] sim_bIn;
    wire [7:0] sim_result;

    float_add test(
        .aIn(sim_aIn),
        .bIn(sim_bIn),
        .result(sim_result)
    );

    initial begin
        sim_aIn = 8'b00000000;
        sim_bIn = 8'b00000000;
        #5
        $display("Output is %b, we
expected %b", sim_result,
8'b00000000);

        sim_aIn = 8'b00001000;
        sim_bIn = 8'b00000011;
        #5
        $display("Output is %b, we
expected %b", sim_result,
8'b00001011);

        sim_aIn = 8'b00110001;
        sim_bIn = 8'b00001100;
        #5
        $display("Output is %b, we
expected %b", sim_result,
8'b00110111);

        sim_aIn = 8'b10010010;
        sim_bIn = 8'b01011111;
        #5
        $display("Output is %b, we
expected %b", sim_result,
8'b10011001);

        sim_aIn = 8'b00011110;
        sim_bIn = 8'b00011000;
        #5
        $display("Output is %b, we
expected %b", sim_result,
8'b00111011);

        sim_aIn = 8'b11111110;
        sim_bIn = 8'b11111000;
        #5
        $display("Output is %b, we
expected %b", sim_result,
8'b11111111);

        sim_aIn = 8'b11111111;
        sim_bIn = 8'b00111111;
        #5
        $display("Output is %b, we
expected %b", sim_result,
8'b11111111);

        sim_aIn = 8'b11111110;
        sim_bIn = 8'b00111111;
        #5
        $display("Output is %b, we
expected %b", sim_result,
8'b11111110);

        $stop;
    end

endmodule
```

big_number_first_tb.v

```
module big_number_first_tb ();

    reg [7:0] sim_aIn, sim_bIn;
    wire [7:0] sim_aOut, sim_bOut;

    big_number_first test (
        .aIn(sim_aIn),
        .bIn(sim_bIn),
        .aOut(sim_aOut),
        .bOut(sim_bOut)
    );

    initial begin
        sim_aIn = 8'b00001000;
        sim_bIn = 8'b00000011;
        #5
        $display("Output is %b and %b,
we expected %b and %b",
sim_aOut, sim_bOut, sim_aIn,
sim_bIn);

        sim_aIn = 8'b00000011;
        sim_bIn = 8'b00001000;
        #5
        $display("Output is %b and %b,
we expected %b and %b",
sim_aOut, sim_bOut, sim_bIn,
sim_aIn);

        sim_aIn = 8'b00110001;
        sim_bIn = 8'b00001100;
        #5
        $display("Output is %b and %b,
we expected %b and %b",
sim_aOut, sim_bOut, sim_aIn,
sim_bIn);

        sim_aIn = 8'b00001100;
        sim_bIn = 8'b00110001;
        #5
        $display("Output is %b and %b,
we expected %b and %b",
sim_aOut, sim_bOut, sim_bIn,
sim_aIn);

        sim_aIn = 8'b11111110;
        sim_bIn = 8'b11111111;
        #5
        $display("Output is %b and %b,
we expected %b and %b",
sim_aOut, sim_bOut, sim_bIn,
sim_aIn);

        sim_aIn = 8'b11111111;
        sim_bIn = 8'b11111110;
        #5
        $display("Output is %b and %b,
we expected %b and %b",
sim_aOut, sim_bOut, sim_aIn,
sim_bIn);

        sim_aIn = 8'b11011111;
        sim_bIn = 8'b11111111;
        #5
        $display("Output is %b and %b,
we expected %b and %b",
sim_aOut, sim_bOut, sim_bIn,
sim_aIn);

        sim_aIn = 8'b11111111;
        sim_bIn = 8'b11011111;
        #5
        $display("Output is %b and %b,
we expected %b and %b",
sim_aOut, sim_bOut, sim_aIn,
sim_bIn);

        $stop;
    end

endmodule
```

shifter_tb.v

```
module shifter_tb ();

reg [4:0] sim_in;
reg [2:0] sim_distance;
reg sim_direction;
wire [4:0] sim_out;

shifter test (
    .in(sim_in),
    .distance(sim_distance),
    .direction(sim_direction),
    .out(sim_out)
);

initial begin
    sim_in = 5'b11001;
    sim_distance = 3'b000;
    sim_direction = 1'b0;
    #5
    $display("Output is %b, we
expected %b", sim_out,
5'b11001);

    sim_in = 5'b11001;
    sim_distance = 3'b001;
    sim_direction = 1'b0;
    #5
    $display("Output is %b, we
expected %b", sim_out,
5'b10010);

    sim_in = 5'b11001;
    sim_distance = 3'b010;
    sim_direction = 1'b0;
    #5
    $display("Output is %b, we
expected %b", sim_out,
5'b00100);

    sim_in = 5'b11001;
    sim_distance = 3'b011;
    sim_direction = 1'b0;
    #5
    $display("Output is %b, we
expected %b", sim_out,
5'b01000);

    sim_in = 5'b11001;
    sim_distance = 3'b100;
    sim_direction = 1'b0;
    #5
    $display("Output is %b, we
expected %b", sim_out,
5'b10000);

    sim_in = 5'b11001;
    sim_distance = 3'b101;
    sim_direction = 1'b0;
    #5
    $display("Output is %b, we
expected %b", sim_out,
5'b00000);

    sim_in = 5'b11001;
    sim_distance = 3'b000;
    sim_direction = 1'b1;
    #5
    $display("Output is %b, we
expected %b", sim_out,
5'b11001);

    sim_in = 5'b11001;
    sim_distance = 3'b001;
    sim_direction = 1'b1;
    #5
    $display("Output is %b, we
expected %b", sim_out,
5'b01100);

    sim_in = 5'b11001;
    sim_distance = 3'b010;
    sim_direction = 1'b1;
    #5
    $display("Output is %b, we
expected %b", sim_out,
5'b00110);
```

shifter_tb.v (continued)

```
sim_in = 5'b11001;
sim_distance = 3'b011;
sim_direction = 1'b1;
#5
$display("Output is %b, we
expected %b", sim_out,
5'b00011);

sim_in = 5'b11001;
sim_distance = 3'b100;
sim_direction = 1'b1;
#5
$display("Output is %b, we
expected %b", sim_out,
5'b00001);

sim_in = 5'b11001;
sim_distance = 3'b101;
sim_direction = 1'b1;
#5
$display("Output is %b, we
expected %b", sim_out,
5'b00000);

$stop;
end

endmodule
```

adder_tb.v

```
module adder_tb ();

reg [4:0] sim_A;
reg [4:0] sim_B;

wire [4:0] sim_S;
wire sim_Cout;

adder test (
    .A(sim_A),
    .B(sim_B),
    .Cout(sim_Cout),
    .S(sim_S)
);
```

```
initial begin
    sim_A = 5'b0;
    sim_B = 5'b0;

    #5;

    $display("Sum is %b, we
expected %b", sim_S, 5'b0);
    $display("Cout is %b, we
expected %b", sim_Cout, 1'b0);

    sim_A = 5'b00001;
    sim_B = 5'b00010;

    #5;

    $display("Sum is %b, we
expected %b", sim_S, 5'b00011);
    $display("Cout is %b, we
expected %b", sim_Cout, 1'b0);

    sim_A = 5'b00111;
    sim_B = 5'b00111;

    #5;

    $display("Sum is %b, we
expected %b", sim_S, 5'b01110);
    $display("Cout is %b, we
expected %b", sim_Cout, 1'b0);

    sim_A = 5'b10000;
    sim_B = 5'b11000;

    #5;

    $display("Sum is %b, we
expected %b", sim_S, 5'b01000);
    $display("Cout is %b, we
expected %b", sim_Cout, 1'b1);

    $stop;
end

endmodule
```